

CHAPTER 3.

Signal Conditioning

3.1 Signal conditioning

3.1.1 Signal conditioning process

- 1. Protection to prevent damage to the next element
- 2. Getting the signal into the right type of signal.
 - Making the signal into a D.C. voltage or current.
- 3. Getting the level of the signal right
 - Amplification
- 4. Eliminating or reducing noise
 - filters
- 5. Signal manipulation
 - Making it a linear function of some variable

3.2 The Operational amplifier

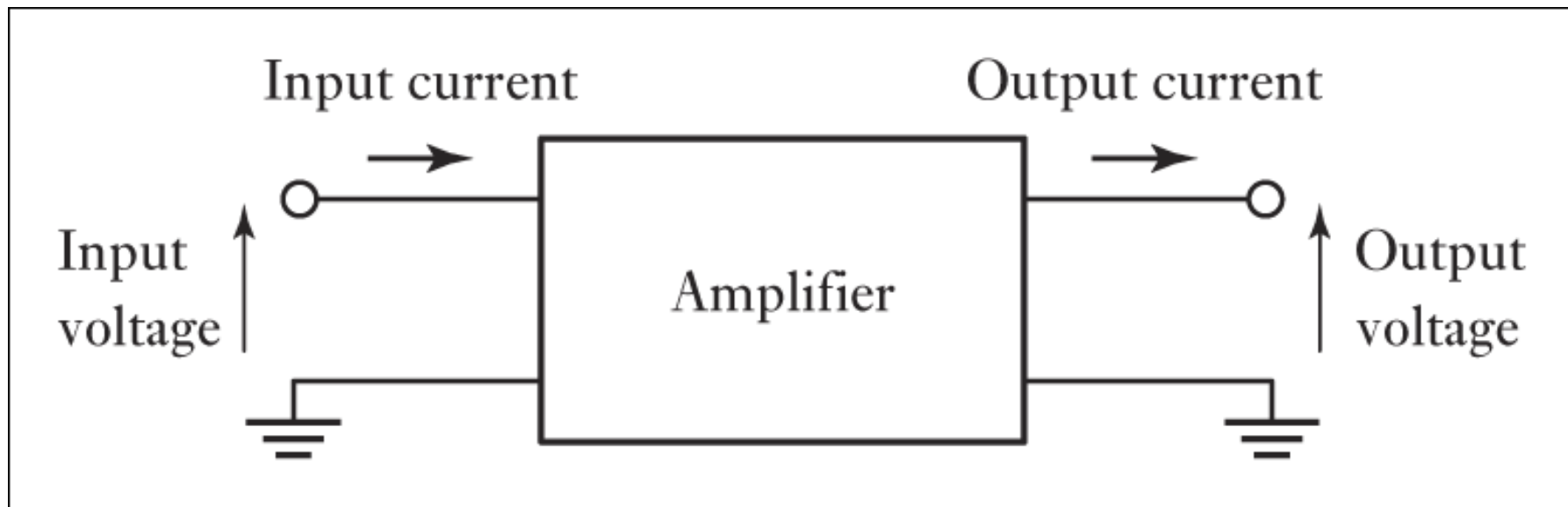


Figure 3.1 Amplifier

3.2 The Operational amplifier


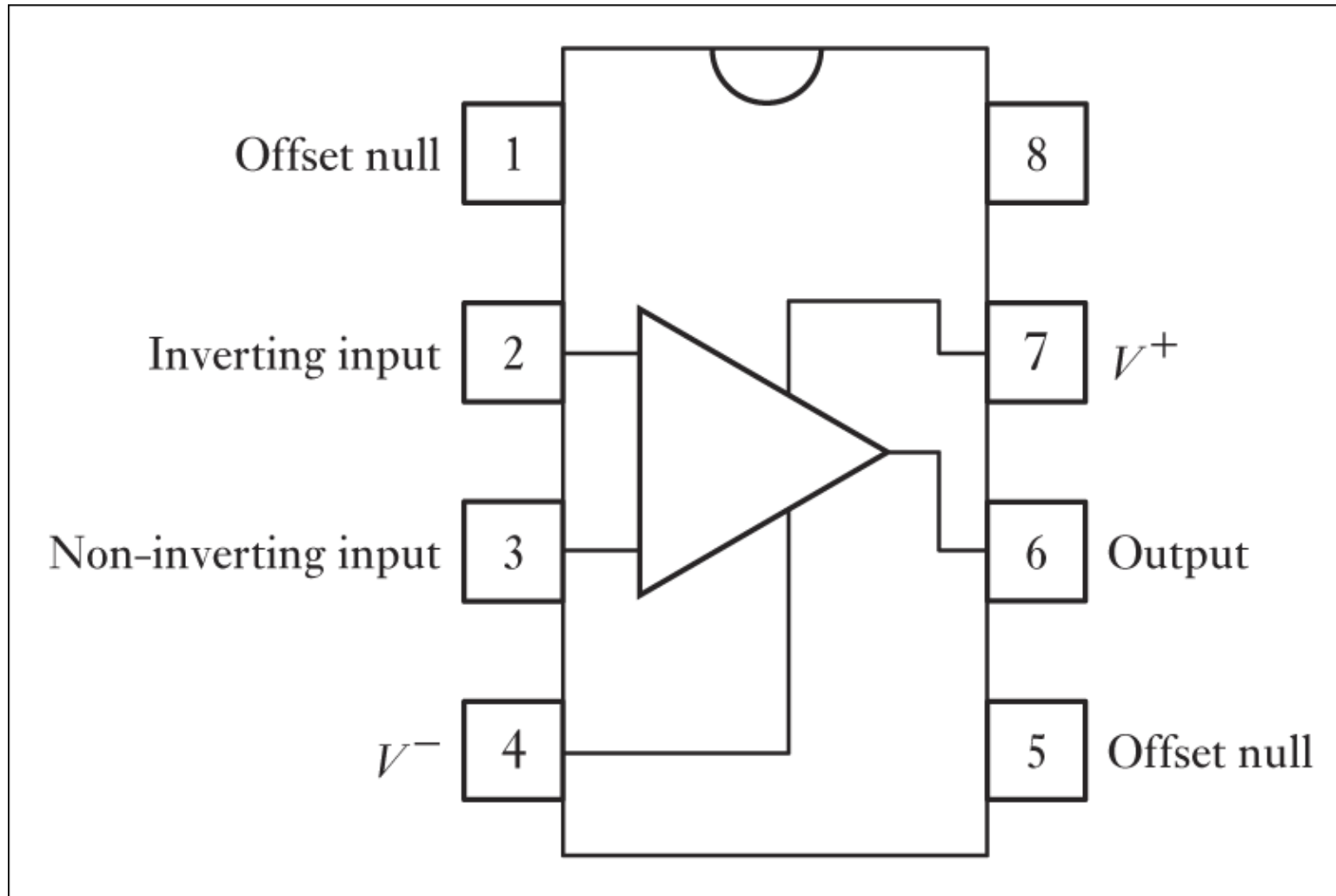


Figure 3.2 Pin connections for a 741-type operational amplifier

3.2.1 Inverting amplifier

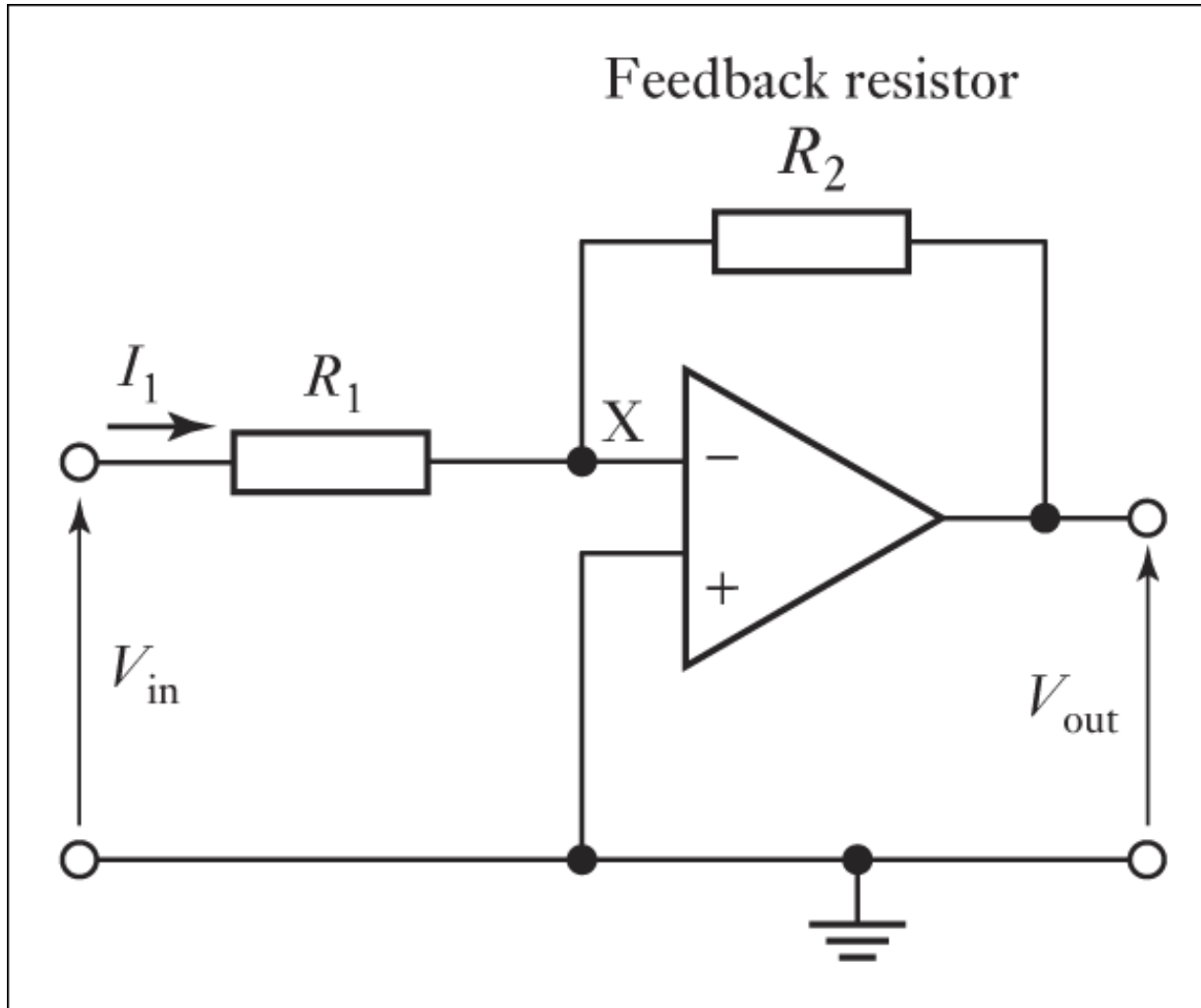

$$V_{in} = I_1 R_1$$

$$-V_{out} = I_1 R_2$$

Voltage Gain

$$= \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Figure 3.3 Inverting amplifier

3.2.2 Non-inverting amplifier

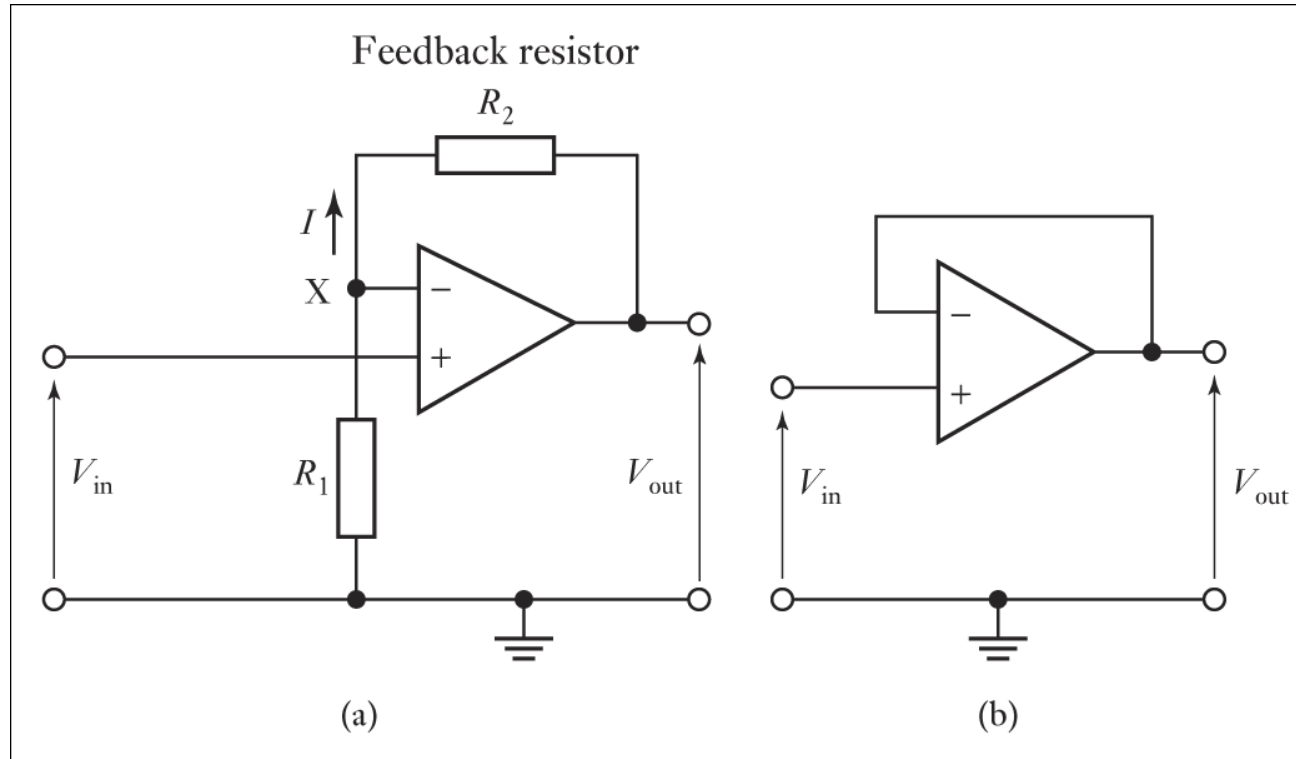


Figure 3.4 (a) Non-inverting amplifier, (b) voltage follower

$$V_X = \frac{R_1}{R_1 + R_2} V_{out}$$

$$\text{Voltage gain} = \frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

3.2.3 Summing amplifier

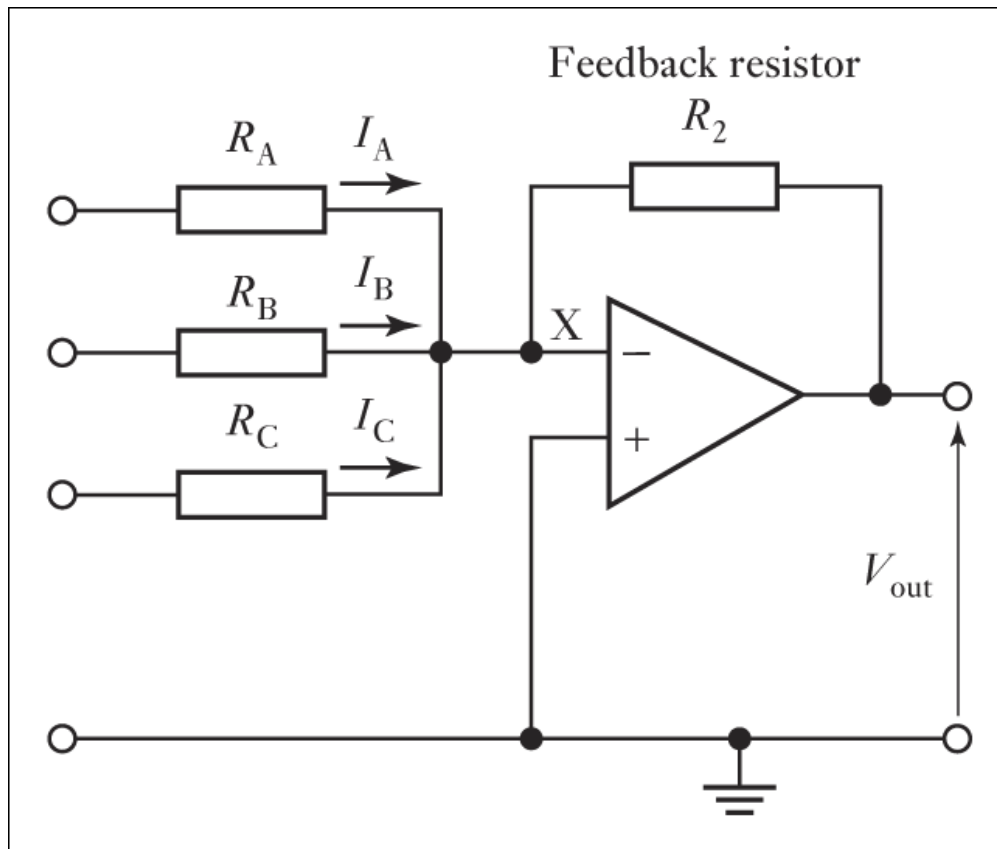


Figure 3.5 Summing amplifier

$$I = I_A + I_B + I_C$$

$$-\frac{V_{out}}{R_2} = \frac{V_A}{R_A} + \frac{V_B}{R_B} + \frac{V_C}{R_C}$$

$$V_{out} = -\left(\frac{R_2}{R_A} V_A + \frac{R_2}{R_B} V_B + \frac{R_2}{R_C} V_C \right)$$

If $R_A = R_B = R_C = R_1$

$$V_{out} = -\frac{R_2}{R_1} (V_A + V_B + V_C)$$

3.2.4 Integrating amplifier

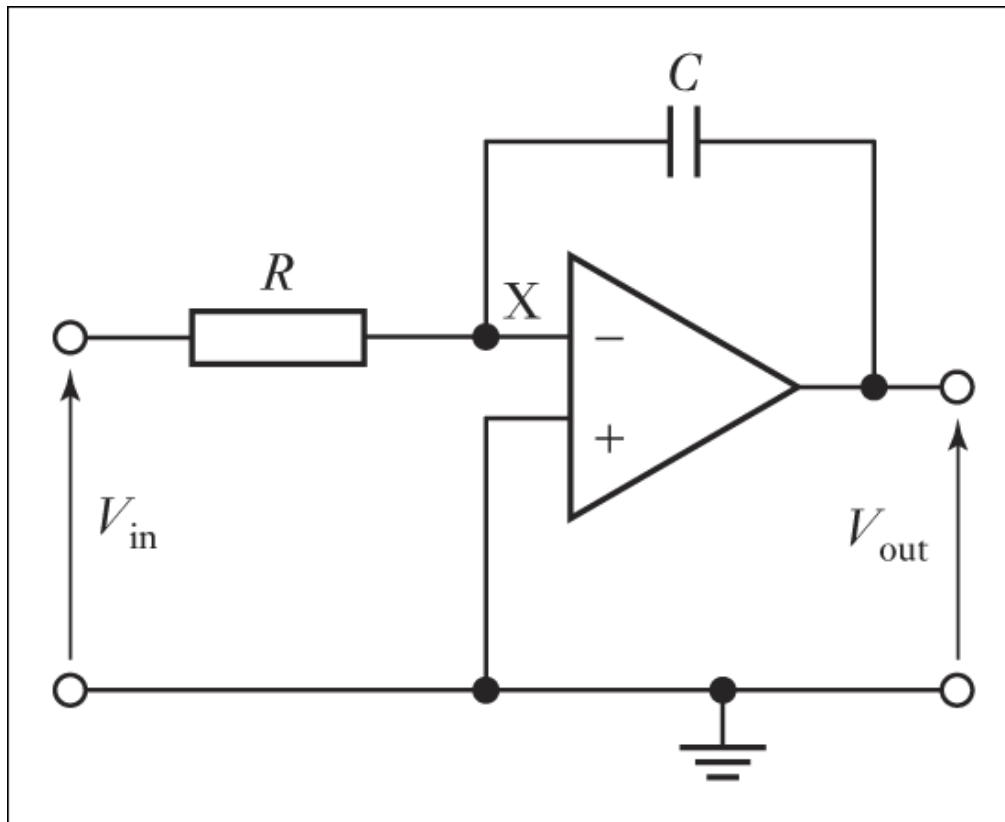


Figure 3.6 Integrating amplifier

$$q = Cv$$


$$i = dq / dt = Cdv / dt$$

$$\frac{v_{in}}{R} = -C \frac{dv_{out}}{dt}$$

$$dv_{out} = -\left(\frac{1}{RC}\right)v_{in}dt$$

$$v_{out}(t_2) - v_{out}(t_1) = -\frac{1}{RC} \int_{t_1}^{t_2} v_{in} dt$$

3.2.5 Difference amplifier

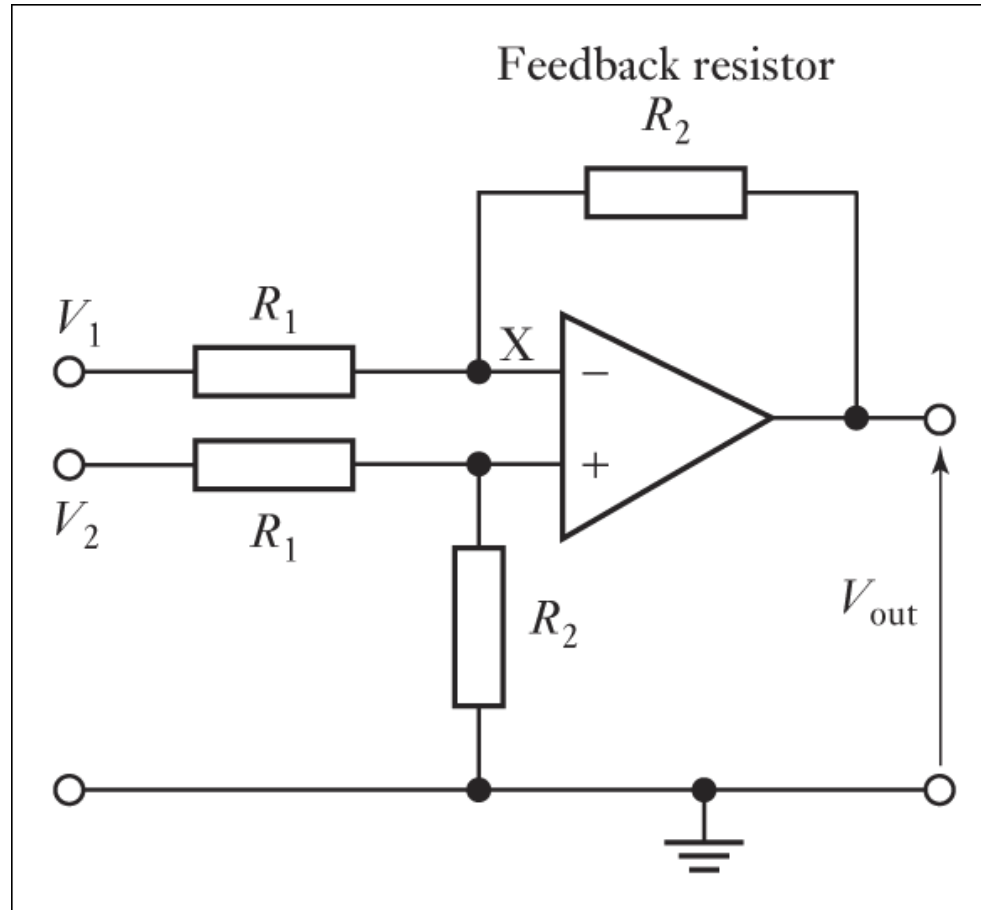

$$\frac{V_X}{V_2} = \frac{R_2}{R_1 + R_2}$$

$$\frac{V_1 - V_X}{R_1} = \frac{V_X - V_{out}}{R_2}$$

$$\frac{V_{out}}{R_2} = V_X \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{V_1}{R_1}$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Figure 3.7 Difference amplifier

3.2.5 Difference amplifier

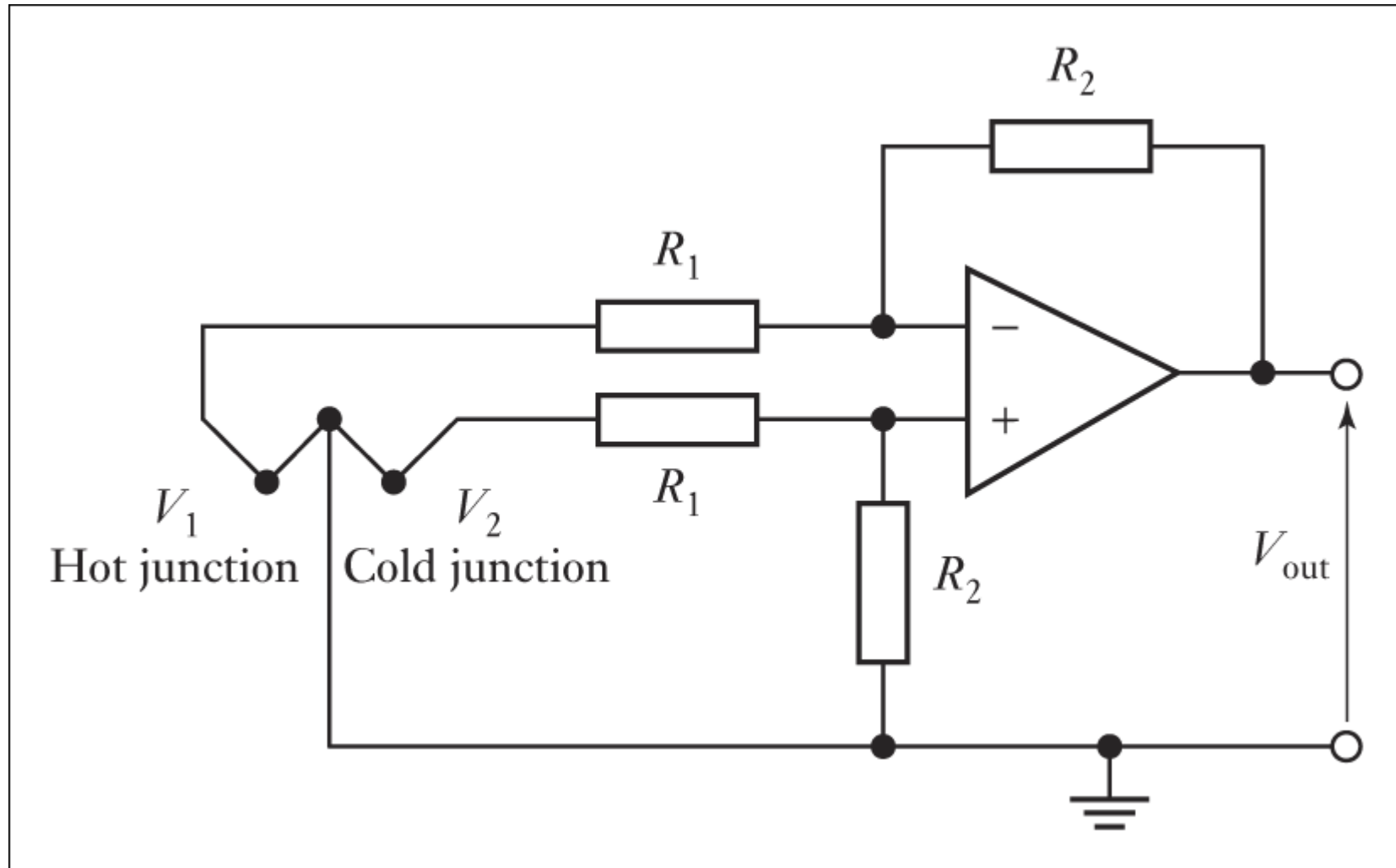


Figure 3.8 Difference amplifier with a thermocouple

3.2.5 Difference amplifier

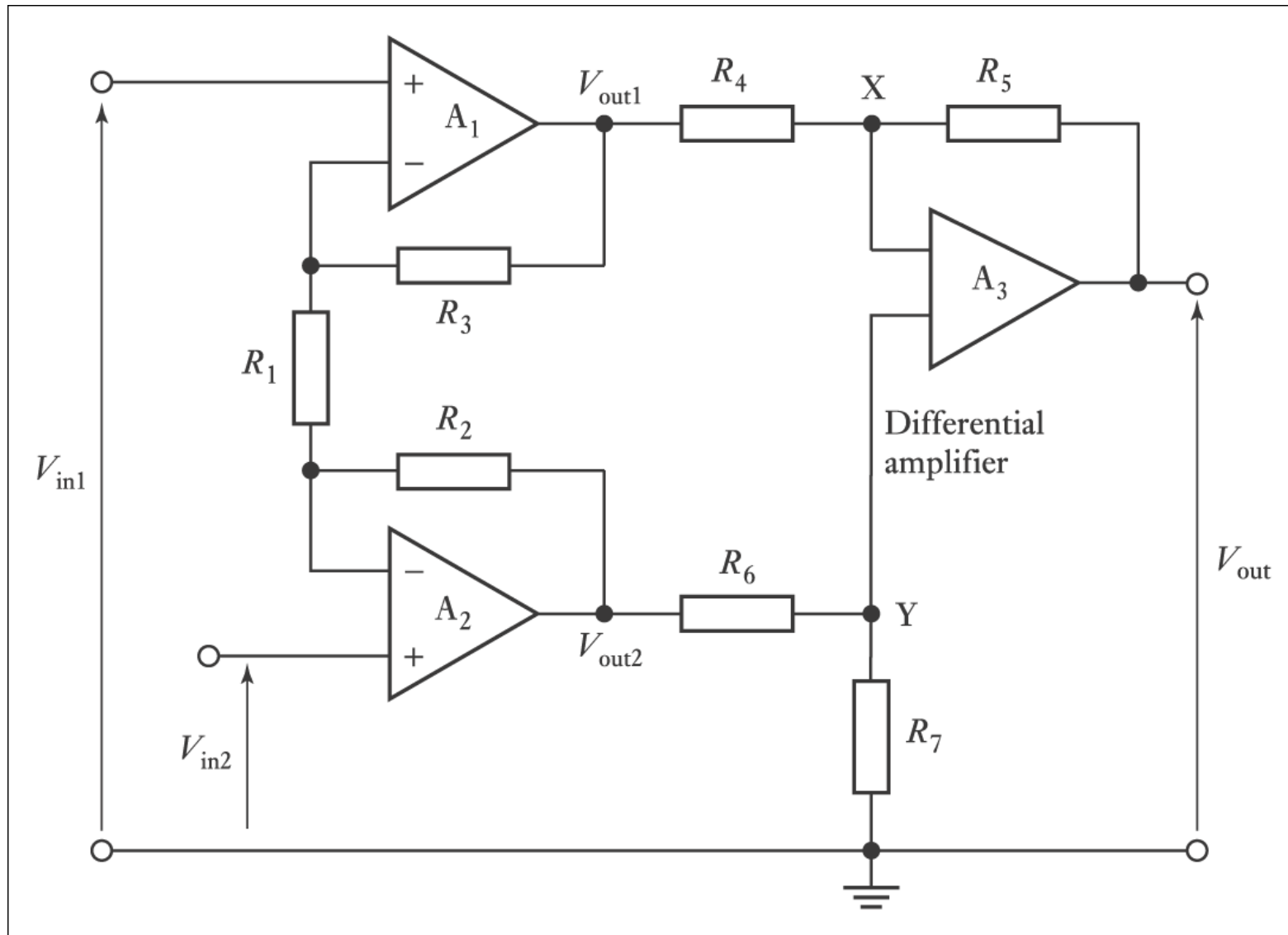


Figure 3.9 Instrumentation amplifier

3.2.5 Difference amplifier

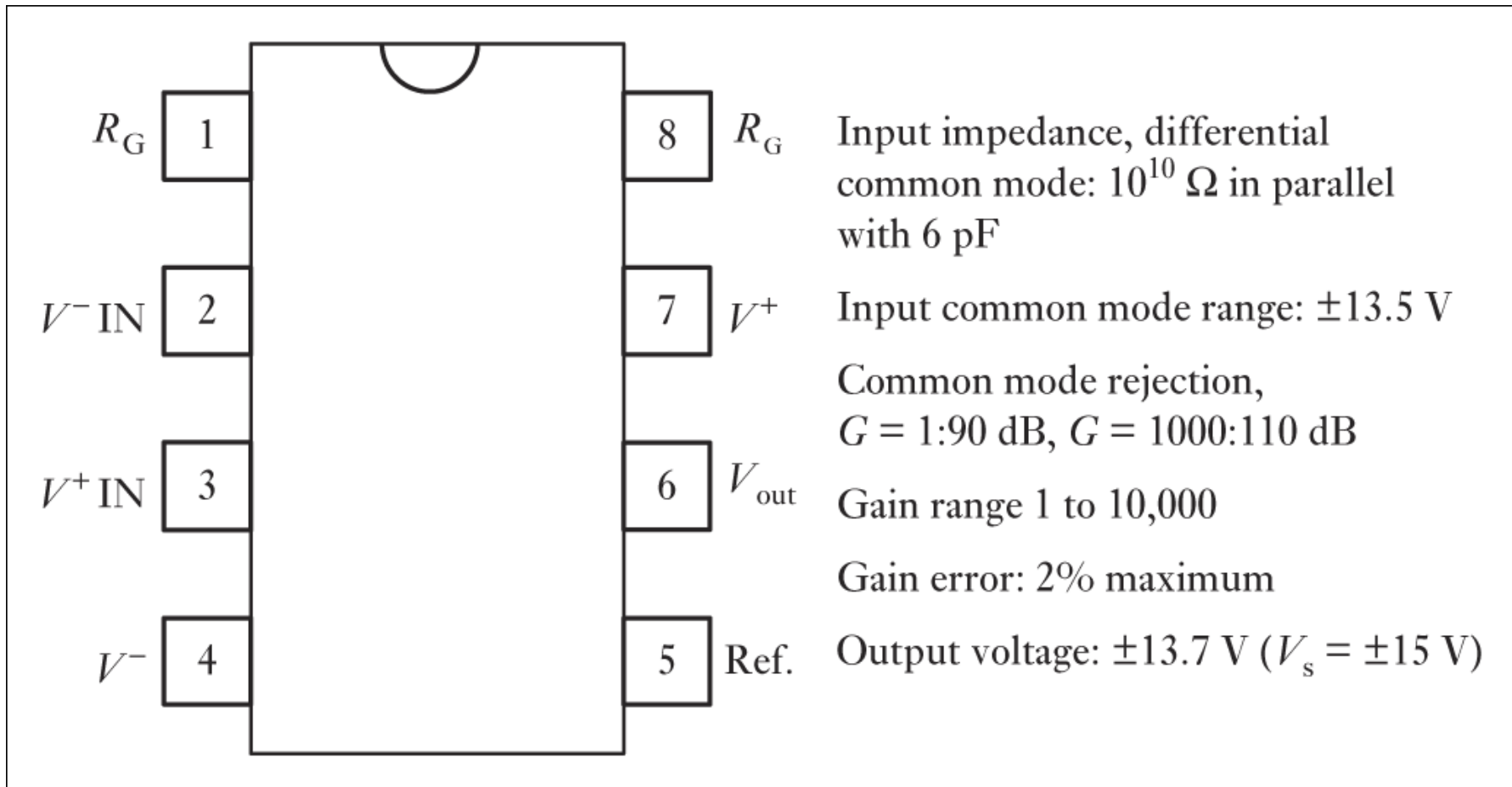


Figure 3.10 INA114

3.2.6 Logarithmic amplifier

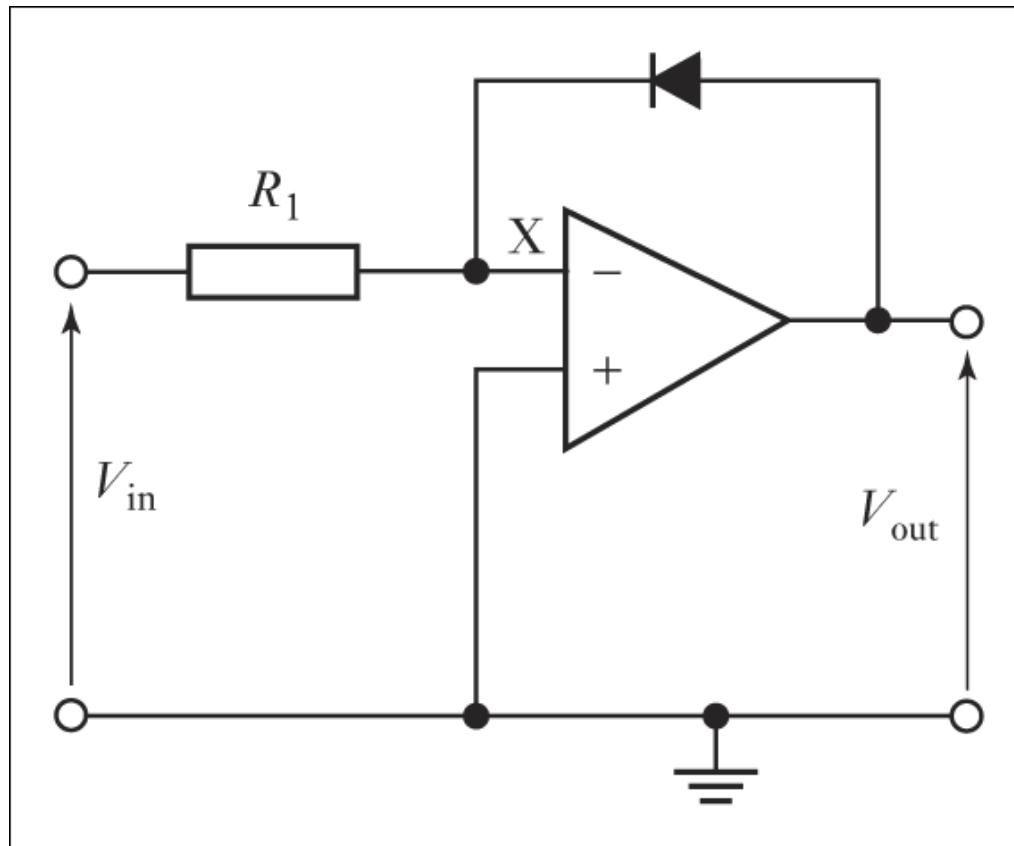


Figure 3.11 Logarithmic amplifier

Diode characteristic

$$V = C \ln I$$

$$V_{out} = -C \ln(V_{in} / R) = K \ln V_{in}$$

If $V_{in} = Ae^{at}$,

$$\begin{aligned} V_{out} &= K \ln V_{in} = K \ln[Ae^{at}] \\ &= K \ln A + Kat \end{aligned}$$

3.2.7 Comparator

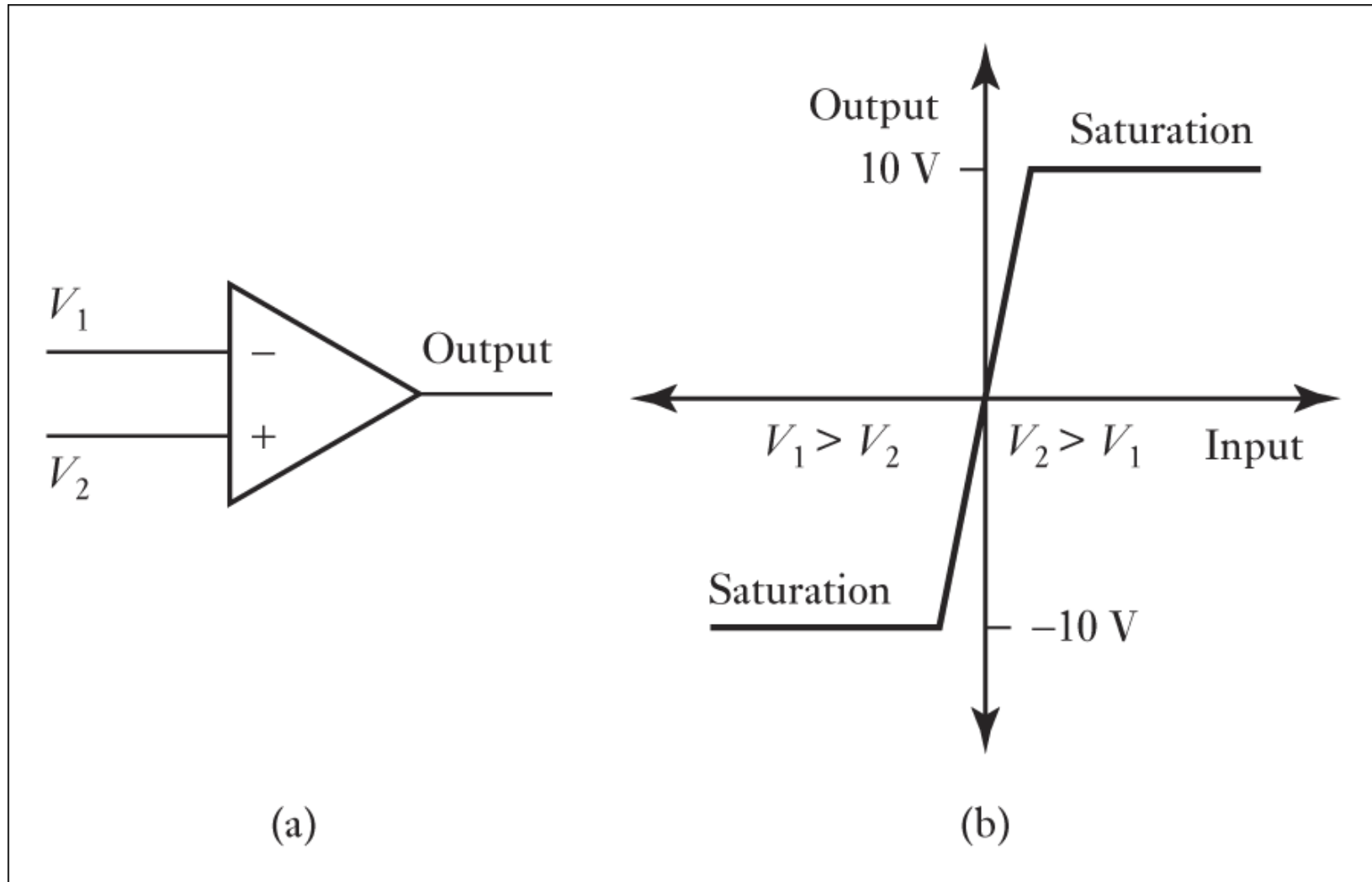


Figure 3.12 Comparator

3.2.7 Comparator

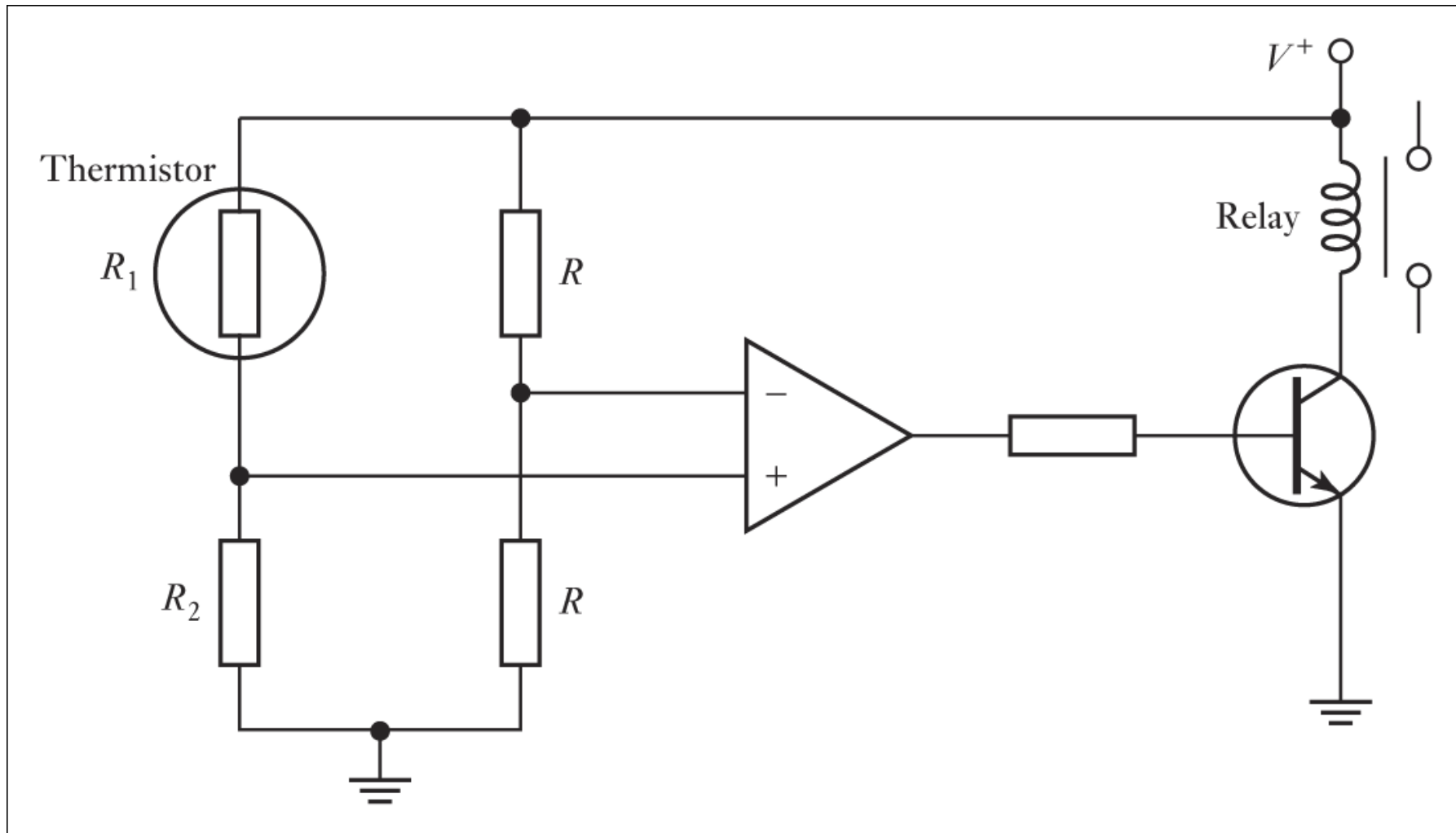


Figure 3.13 Temperature switch circuit

3.2.8 Amplifier errors

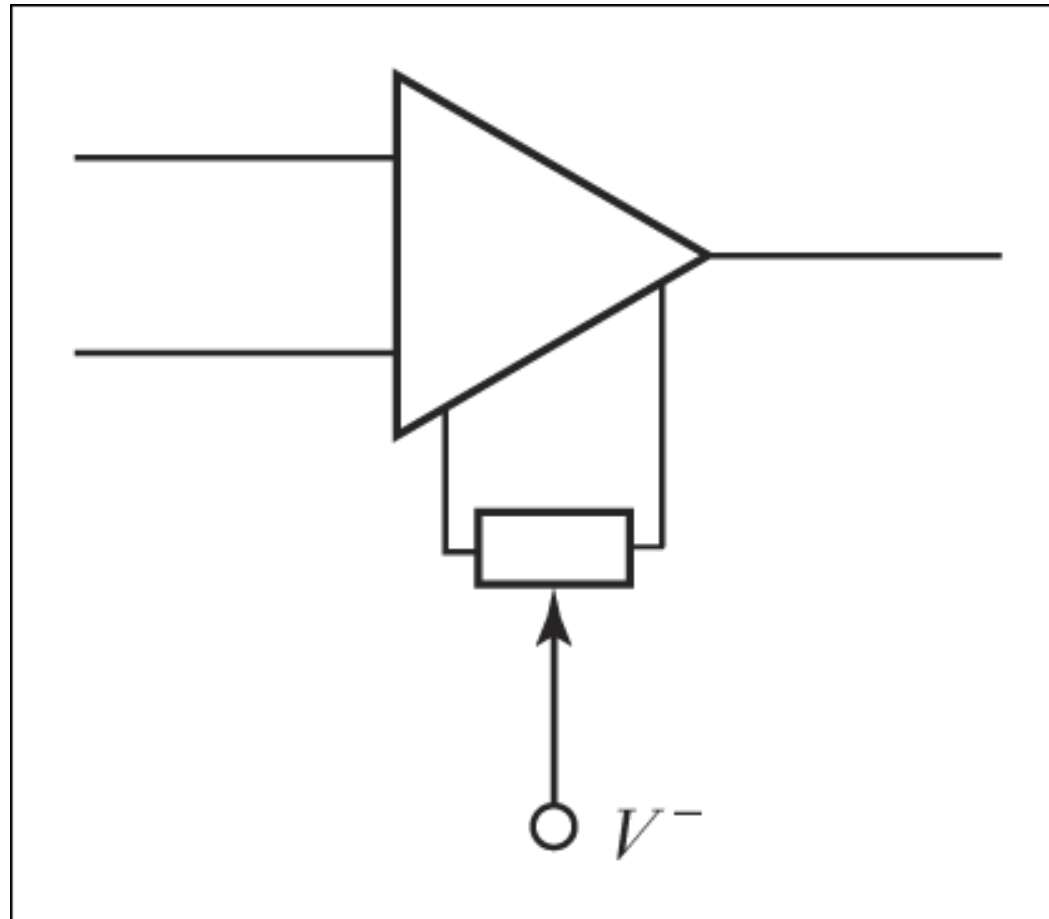


Figure 3.15 Correcting the offset voltage

3.3 Protection

- Limit

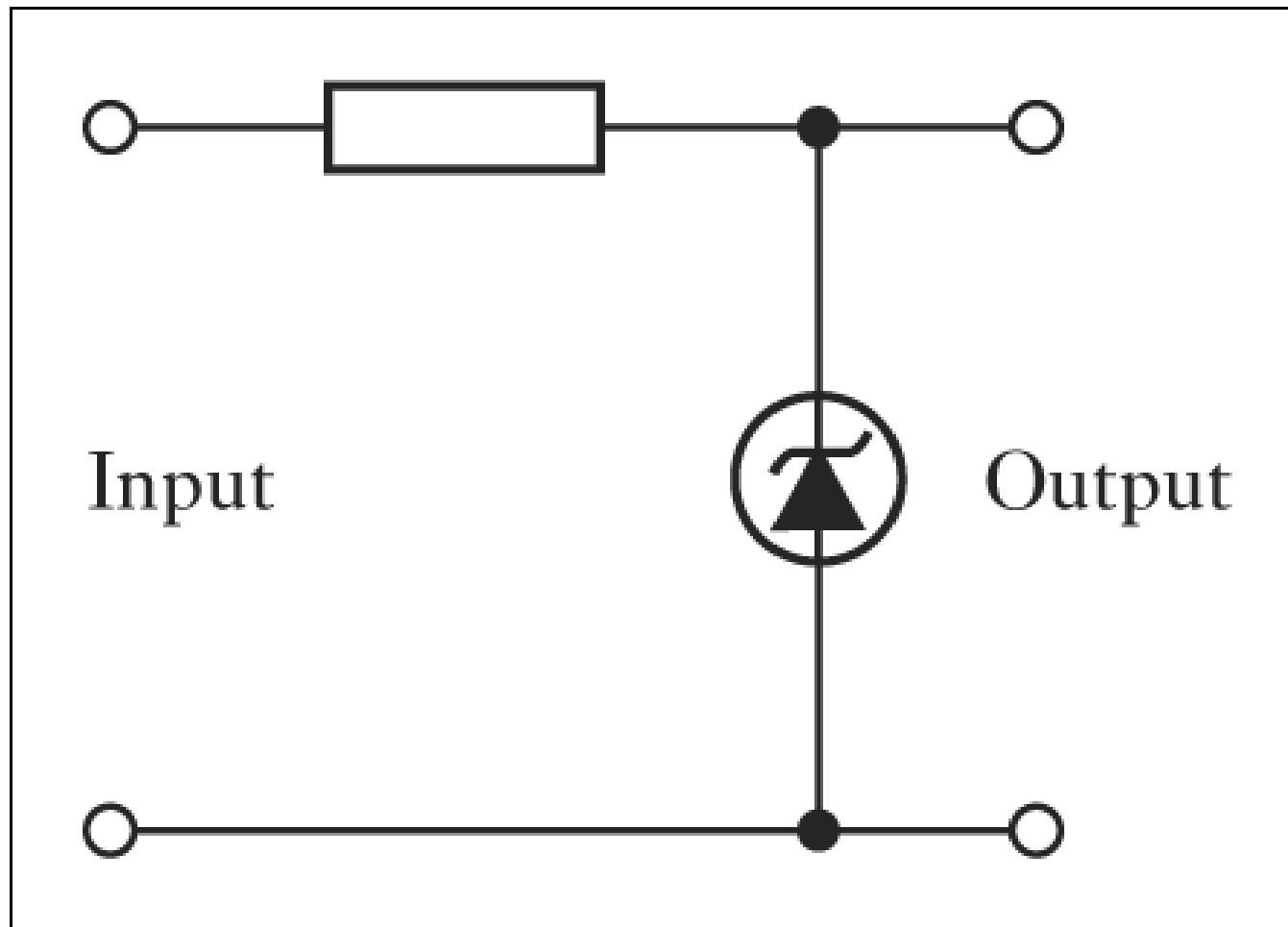


Figure 3.16 Zener diode protection circuit

3.3 Protection

- Isolation

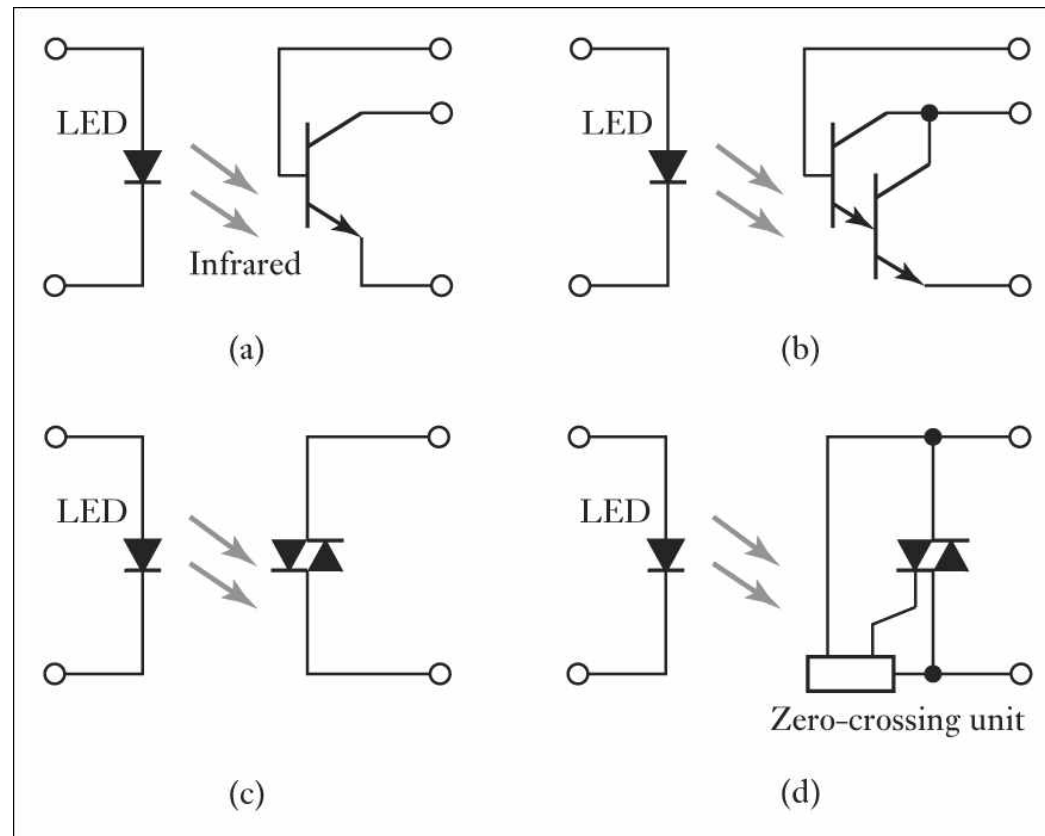


Figure 3.17 Optoisolators: (a) transistor, (b) Darlington, (c) triac, (d) triac with zero-crossing unit

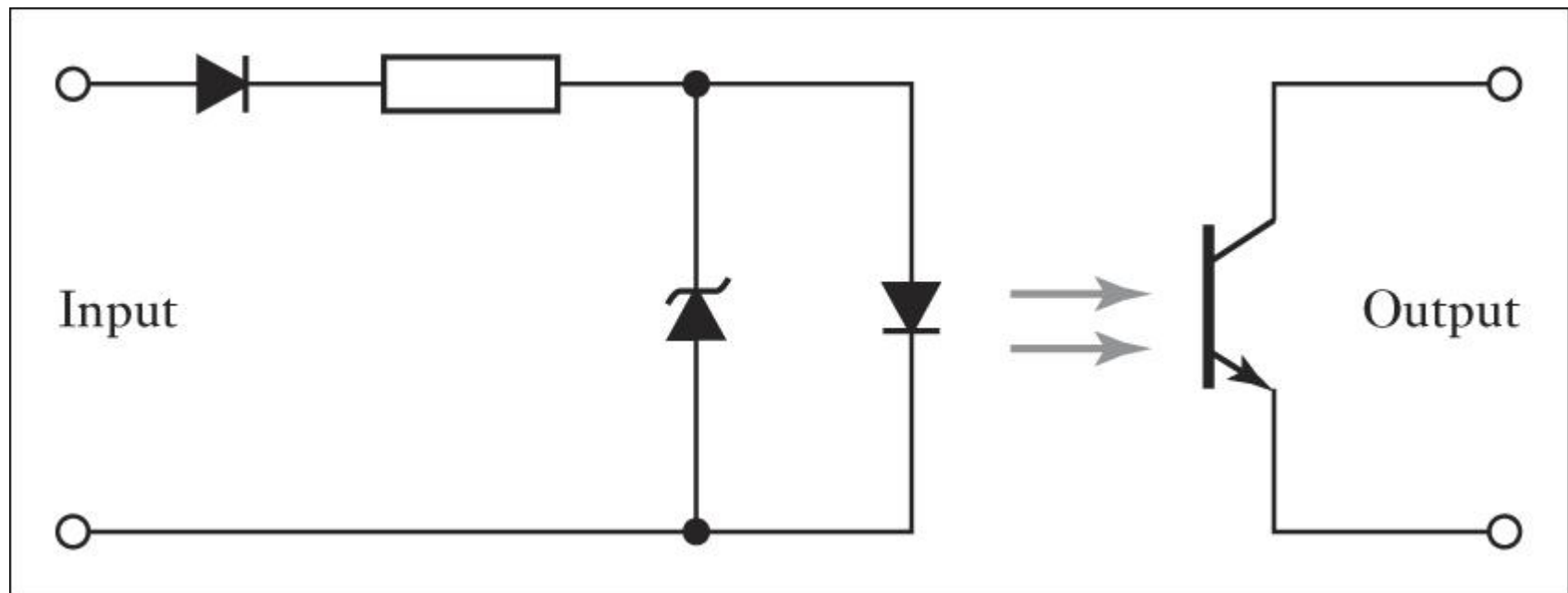


Figure 3.18 Protection circuit

3.4 Filtering

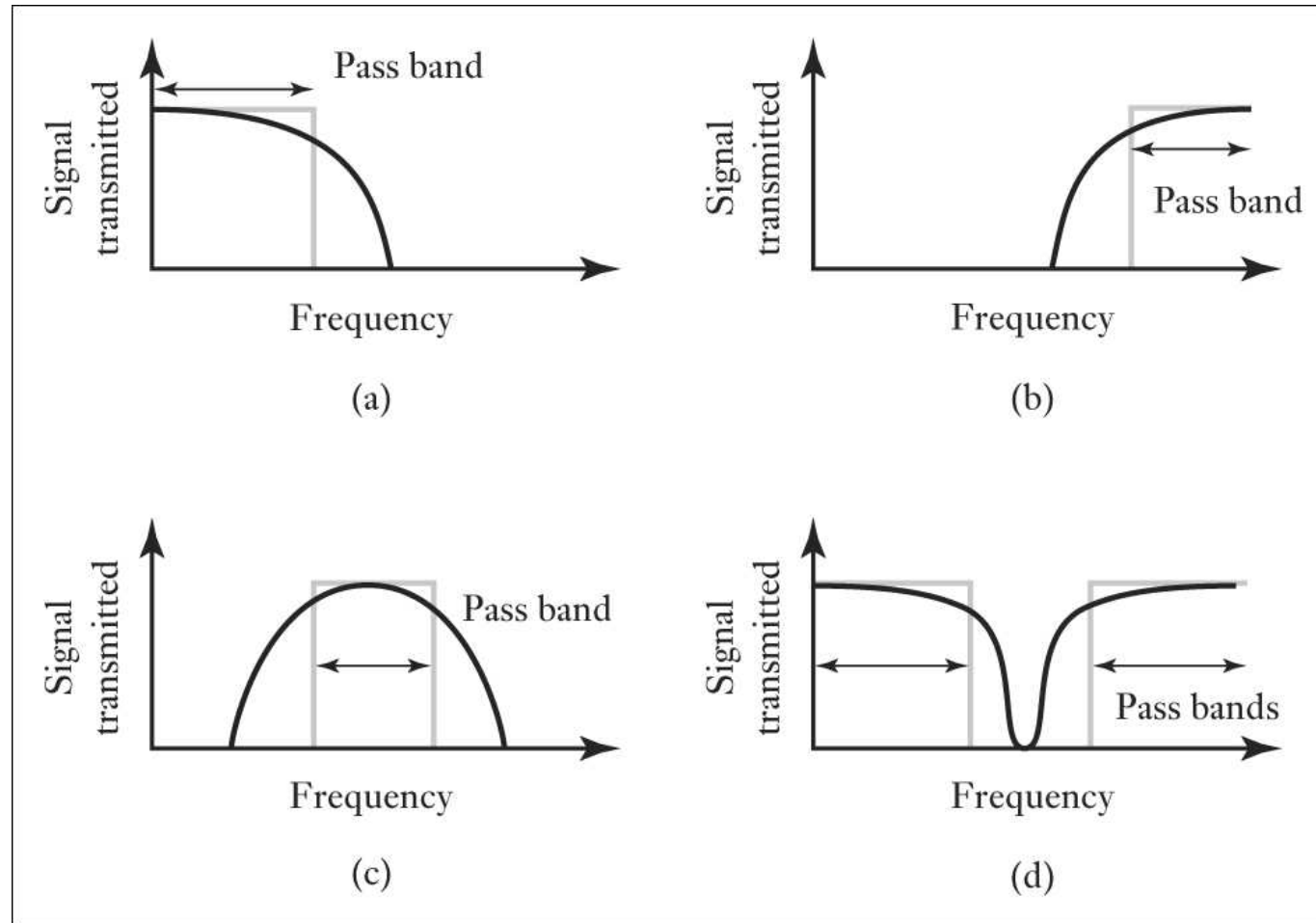


Figure 3.19 Characteristics of ideal filters: (a) low-pass filter, (b) high-pass filter, (c) band-pass filter, (d) band-stop filter

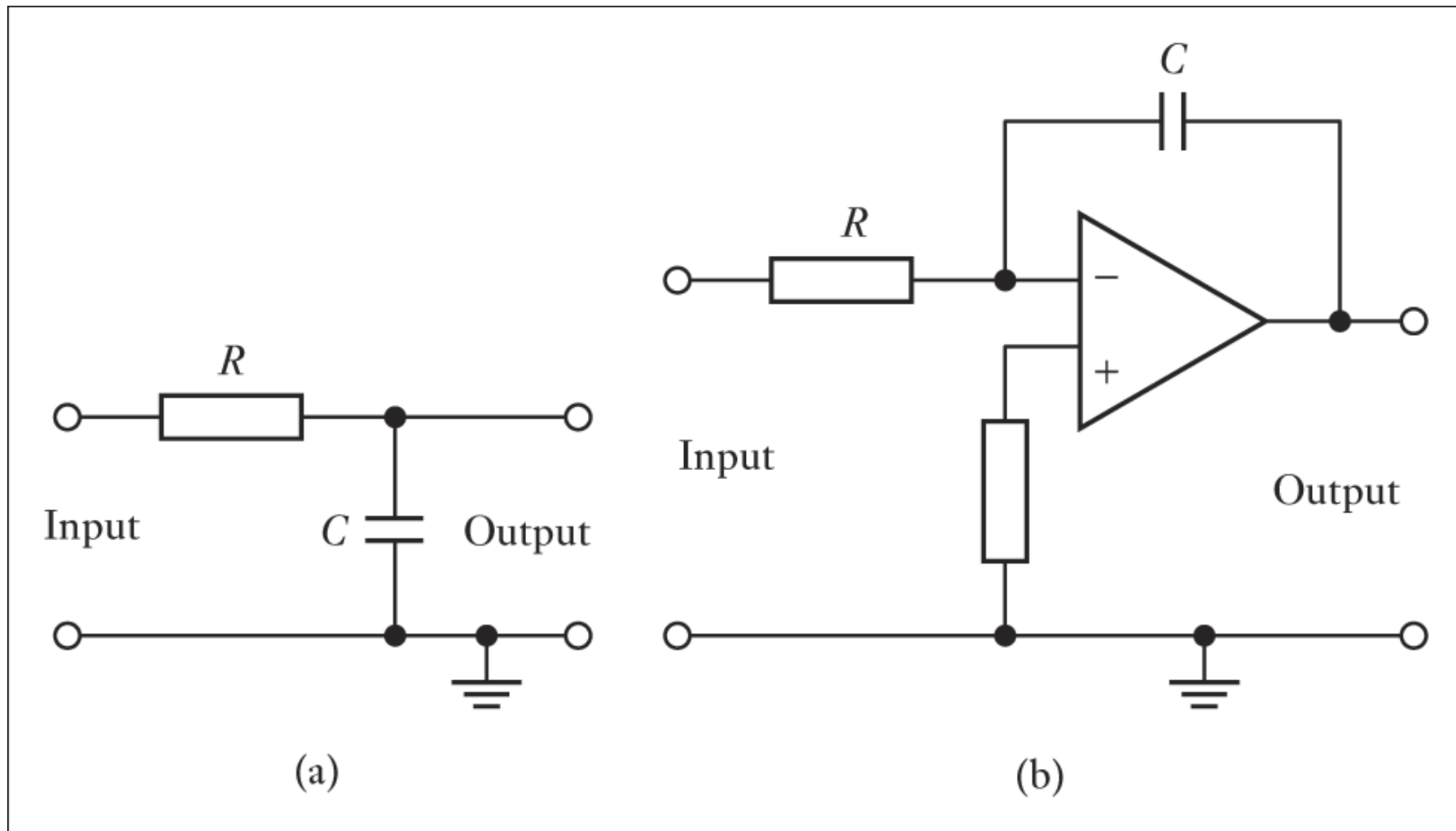


Figure 3.20 Low-pass filter: (a) passive, (b) active using an operational amplifier

3.5 Wheatstone bridge

- Balanced $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

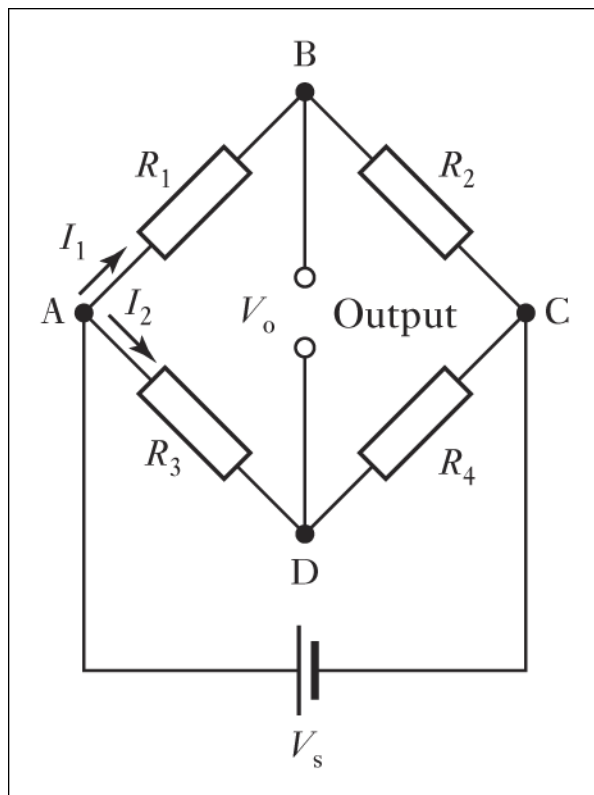


Figure 3.21 Wheatstone bridge

- Output


$$V_{AB} = \frac{V_S R_1}{R_1 + R_2}$$

$$V_{AD} = \frac{V_S R_3}{R_3 + R_4}$$

$$V_o = V_{AB} - V_{AD} = V_s \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

- Output
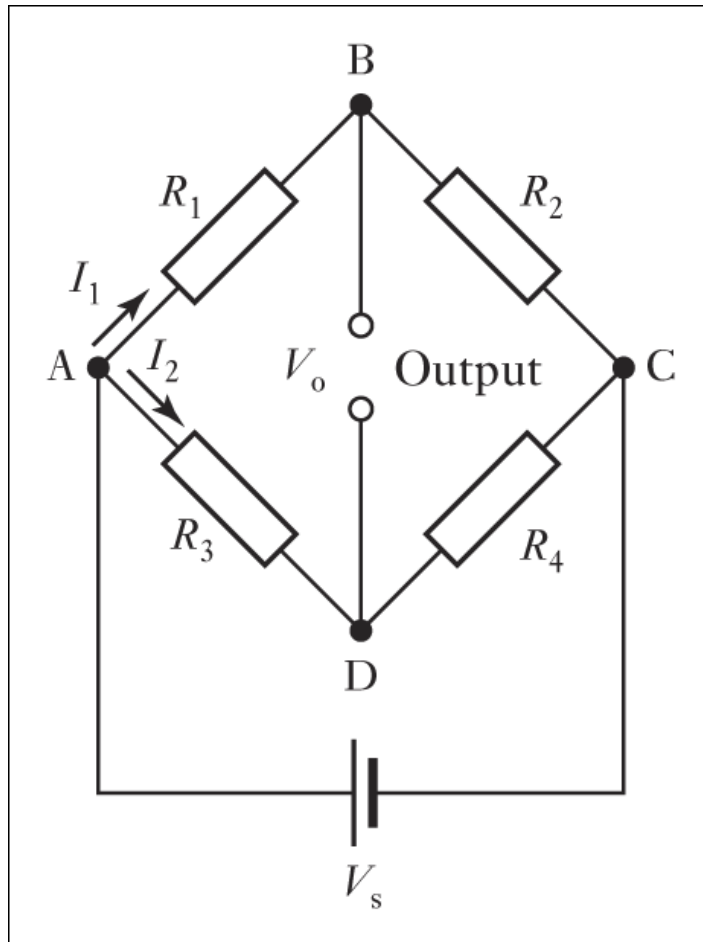
$$V_o = V_{AB} - V_{AD} = V_s \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$



$$V_o + \delta V_o = V_s \left(\frac{R_1 + \delta R_1}{R_1 + \delta R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

$$(V_o + \delta V_o) - V_o = V_s \left(\frac{R_1 + \delta R_1}{R_1 + \delta R_1 + R_2} - \frac{R_1}{R_1 + R_2} \right)$$

$$\delta V_o \approx V_s \left(\frac{\delta R_1}{R_1 + R_2} \right)$$

Figure 3.21 Wheatstone bridge

3.5.1 Temperature compensation

- 3 lead compensation

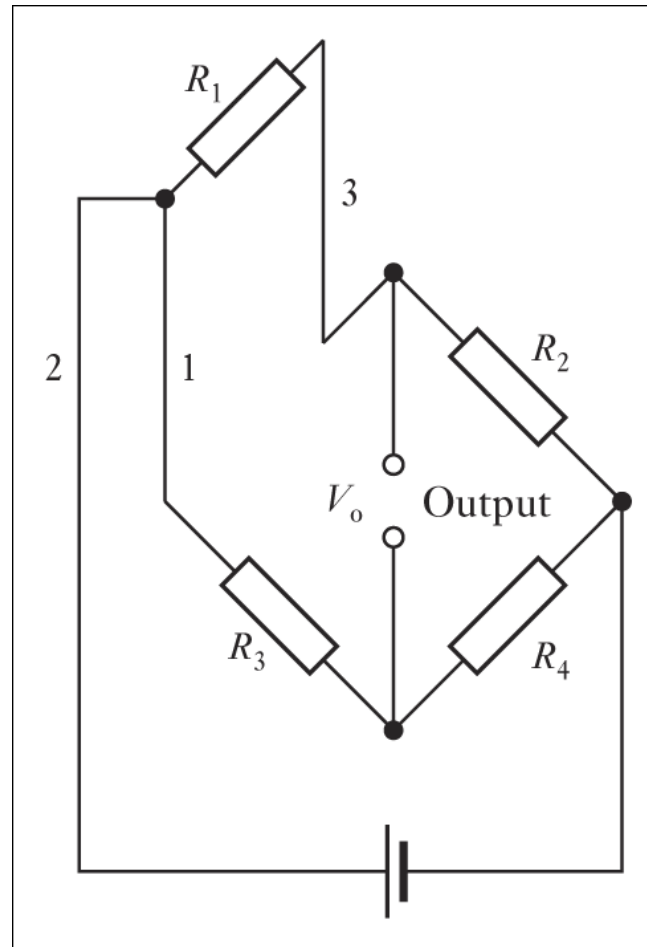


Figure 3.22 Compensation for leads

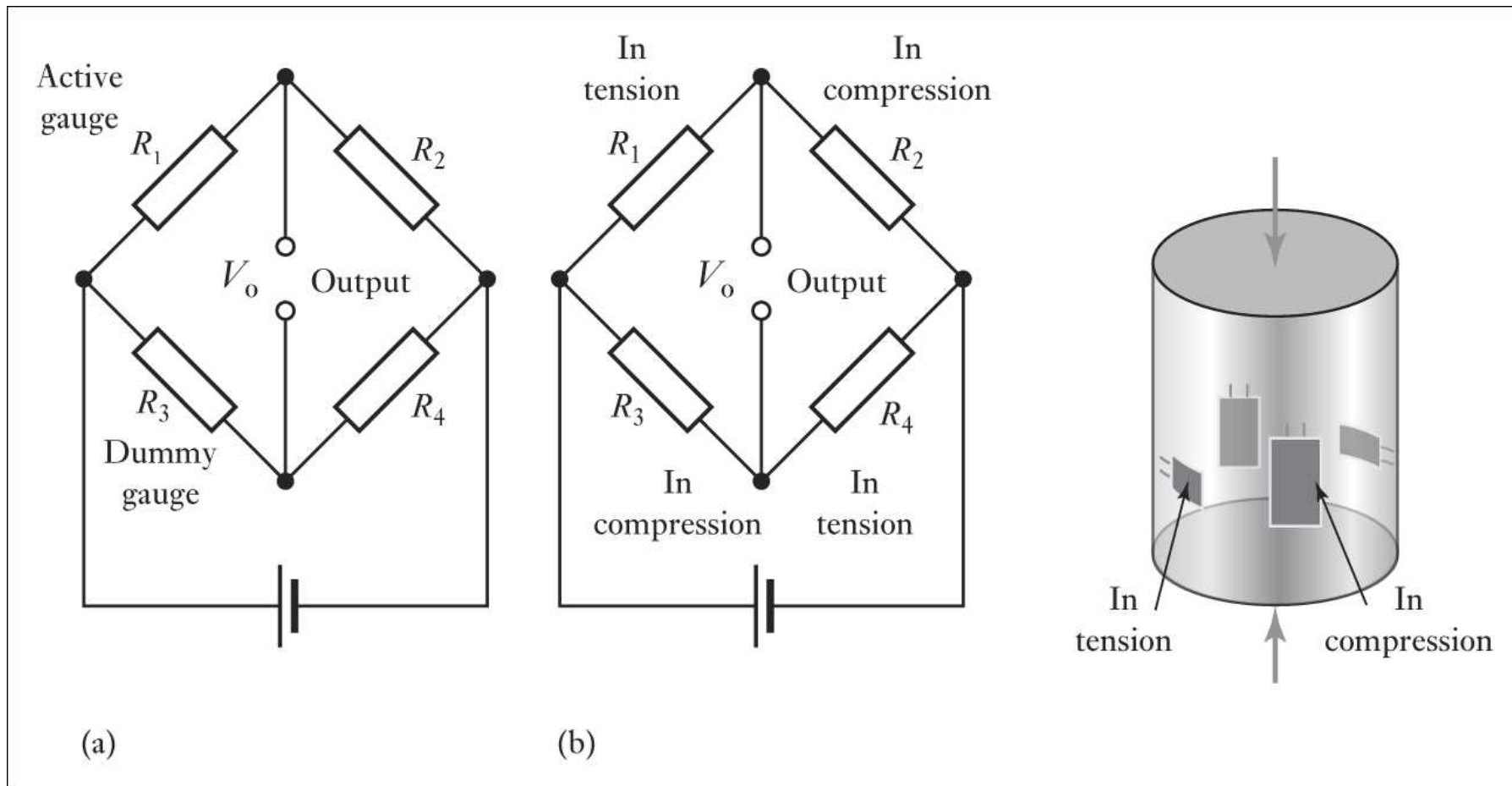


Figure 3.23 Compensation with strain gauges: (a) use of dummy gauge, (b) four active arm bridge

3.6 Pulse modulation

- A problem that is often encountered with dealing with the transmission of low-level D.C. signals from sensors is that the gain of an operational amplifier used to amplify them may drift and so the output drifts.
- This problem can be overcome if the signal is a sequence of pulses rather than a continuous-time signal.

3.6 Pulse modulation

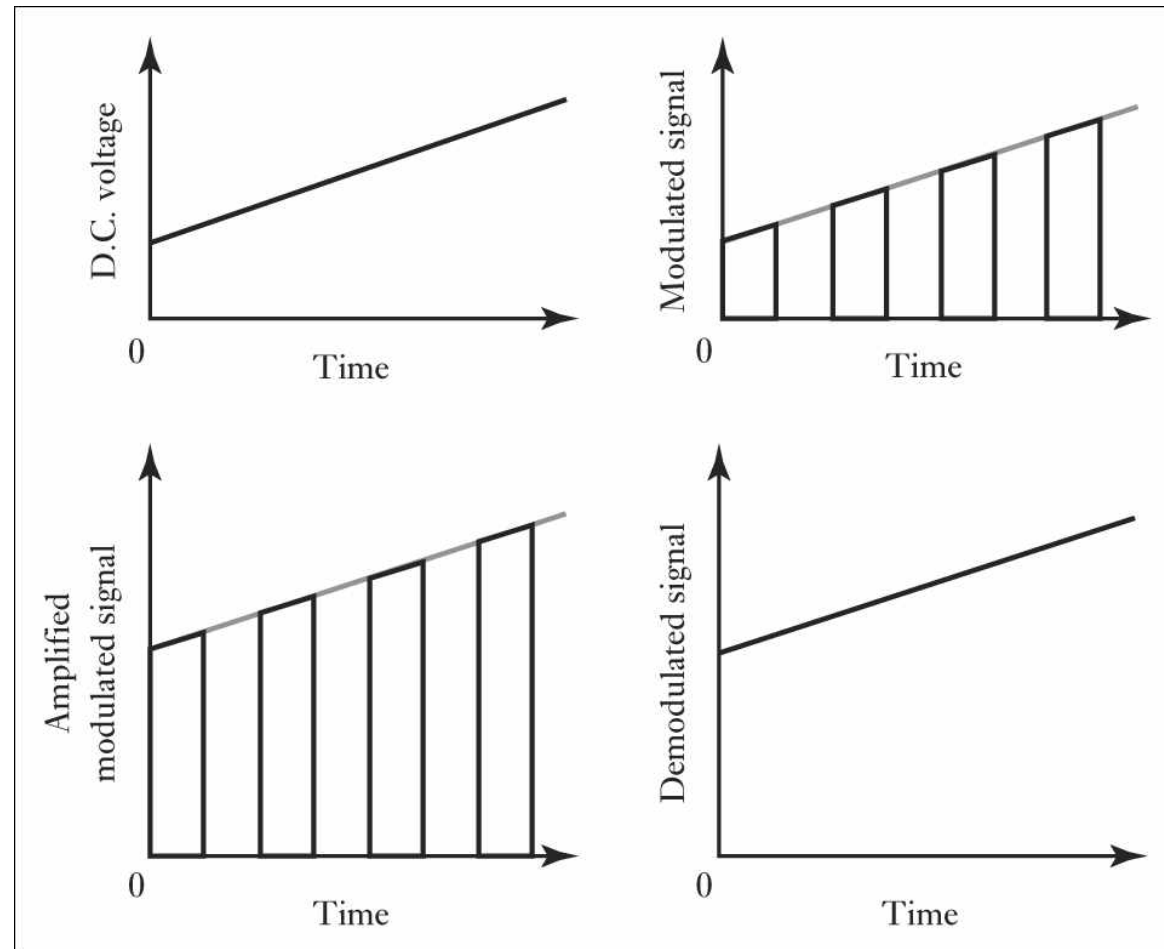


Figure 3.24 Pulse amplitude modulation

3.6 Pulse modulation

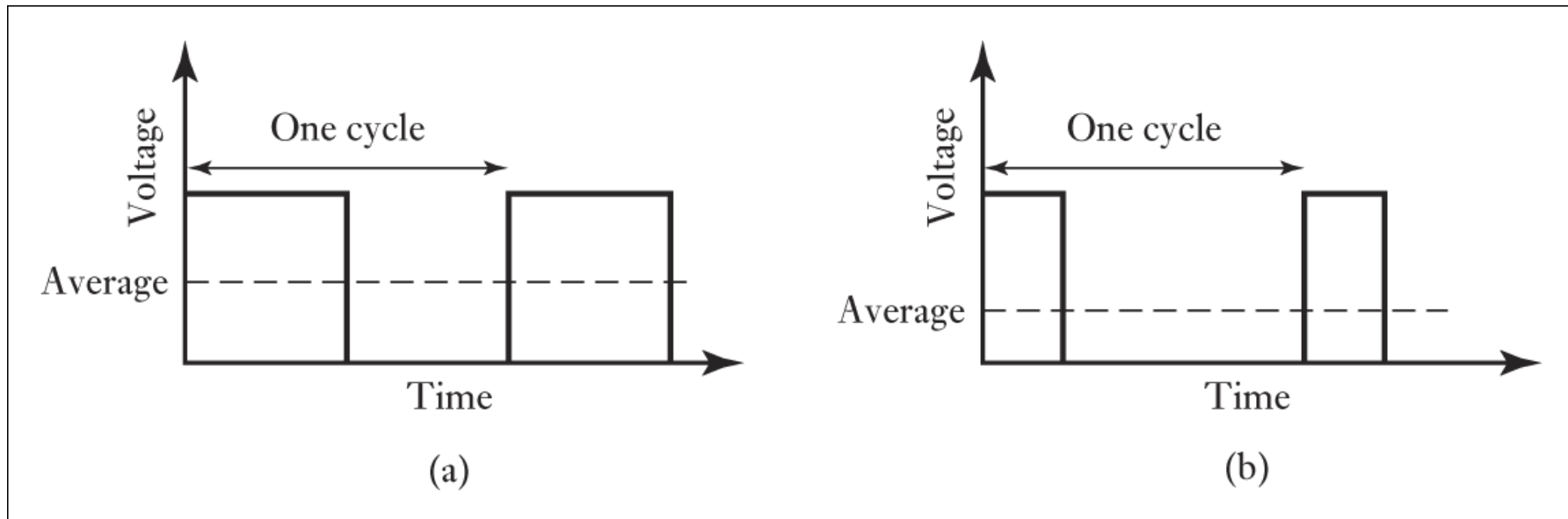


Figure 3.25 PWM for voltage control: (a) duty cycle 50%, (b) duty cycle 25%